


CS1026 II Assignment 7

Write a Verilog behavioural description

```
module OddFunction (output A, input x, y, clk, reset_b);
```

of the circuit below. Test data will change on the falling edge of the clock and your machine should change state on the rising edge.

 
Your design should enter state 0 on the negative edge of the reset signal.



(a) Circuit diagram

Present state	Inputs		Next state
A	x	y	A
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

(b) State table

 

(c) State diagram

